<u>Lab 10</u>


<u>To Design and Implement Multiplexer & Demultiplexer</u>

Tasks

1. Construct a logic circuit for 8 to 1 multiplexer with the help of truth table. Also write the Boolean expression for output(s). Simulate your circuit to verify the outputs.

8 to 1 Mux

a) Block Diagram

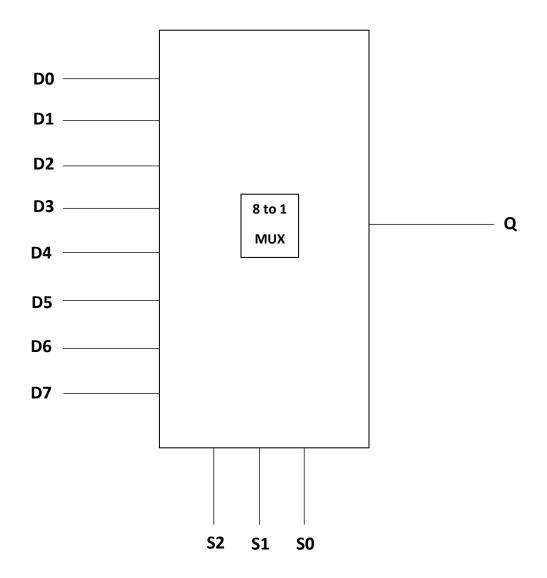


b) Truth Table

S2	S1	S1	Q
0	0	0	D 0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D 5
1	1	0	D6
1	1	1	D7


c) Boolean Expression


Q = S2'.S1'.S0'.D0 + S2'.S1'.S0.D1 + S2'.S1.S0'.D2 + S2'.S1.S0.D3 + S2.S1'.S0'.D4 + S2.S1'.S0.D5 + S2.S1.S0'.D6 + S2.S1.S0.D7

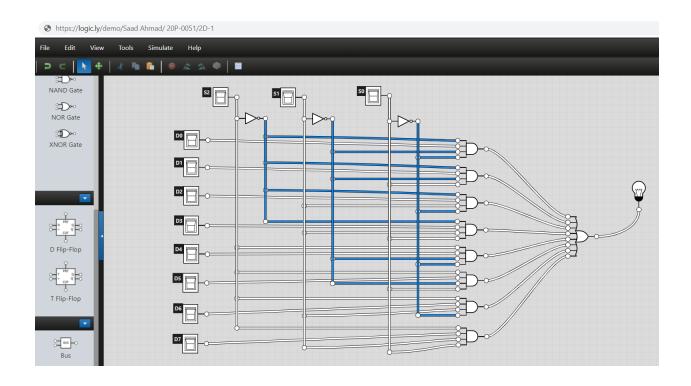d) Logic Diagram (from logicaly or hand drawn)




e) Software Simulation

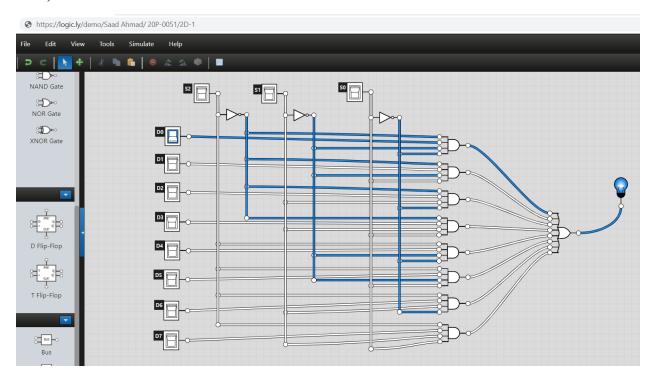

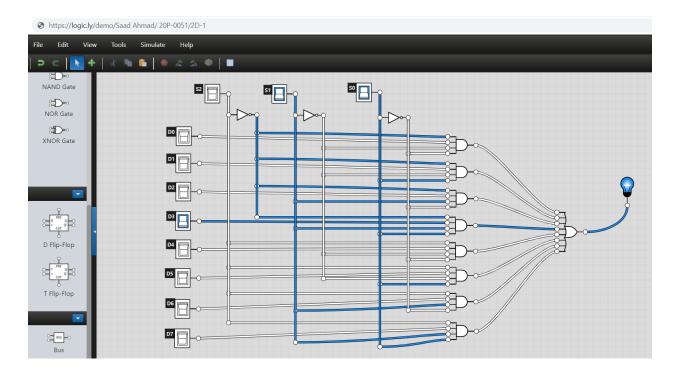

2. Design a logic circuit for 1-to-4-line Demultiplexer. Also write the Boolean expression for output(s). Simulate your circuit to verify the outputs.

a) Block Diagram

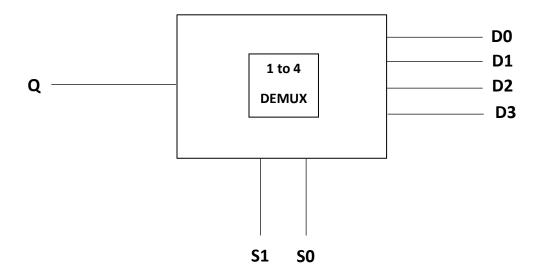

b) Truth Table

S1	S0	Q
0	0	D0
0	1	D1
1	0	D2
1	1	D3

c) Boolean Expression


$$D0 = S1'. S0'. Q$$

$$D1 = S1'. S0. Q$$


$$D2 = S1. S0'. Q$$


$$D3 = S1. S0. Q$$


d) Logic Diagram

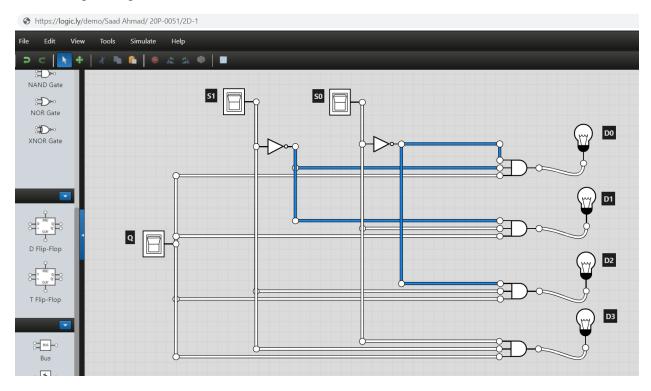


e) Software Simulation

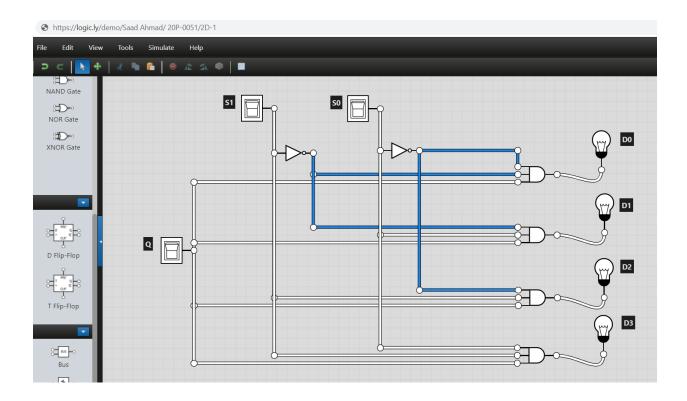

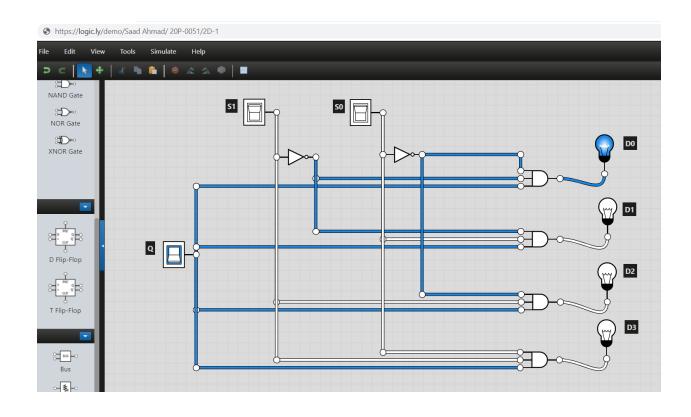

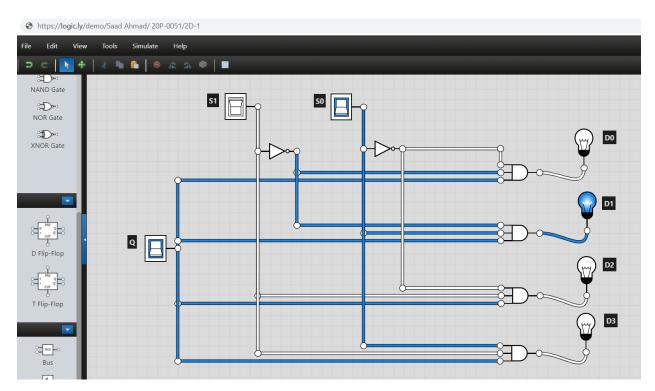

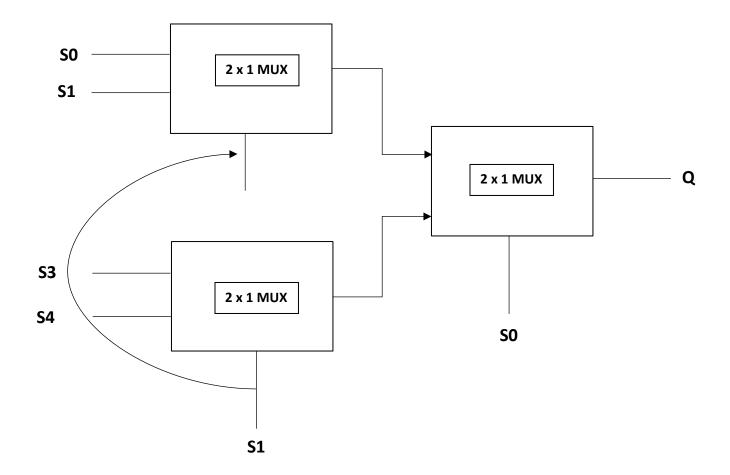- 3. Design a circuit for 4 to 1 Multiplexer using 2 to 1 Multiplexer(s). You can take help from google or the link below. Just ignore the coding language discussed in the link. https://bravelearn.com/design-of-4x2-multiplexer-using-2x1-mux-in-verilog/
- a) Block Diagram



b) Truth Table

S1	S0	Q
0	0	D0
0	1	D1
1	0	D2
1	1	D3

c) Logic Circuit (on the basis of 2 to 1 Muxes used/follow the block diagram to draw this circuit)

You need to connect three 2 x1 Multiplexers in order to make one 4x1 Multiplexer.

