

Lab 6

To Demonstrate the Working of Binary Subtractor

Note: You may draw all the logic diagrams with hand and paste the pictures here or on logicly software with your name, roll number & section mentioned in your workspace. Make sure that all of your connections are clearly visible and distinguishable.

Tasks

1. Construct a logic circuit for half and full subtractor with the help of truth table/Boolean expression. Also write the Boolean expression for output(s).

Half Subtractor

a) Truth Table

A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

b) Boolean Expression (Simplified)


Difference:

$$D = A \text{ X-OR } B = A \oplus B$$


Borrow:


$$B = \text{NOT } A \text{ AND } B = A' . B$$

c) Logic Diagram

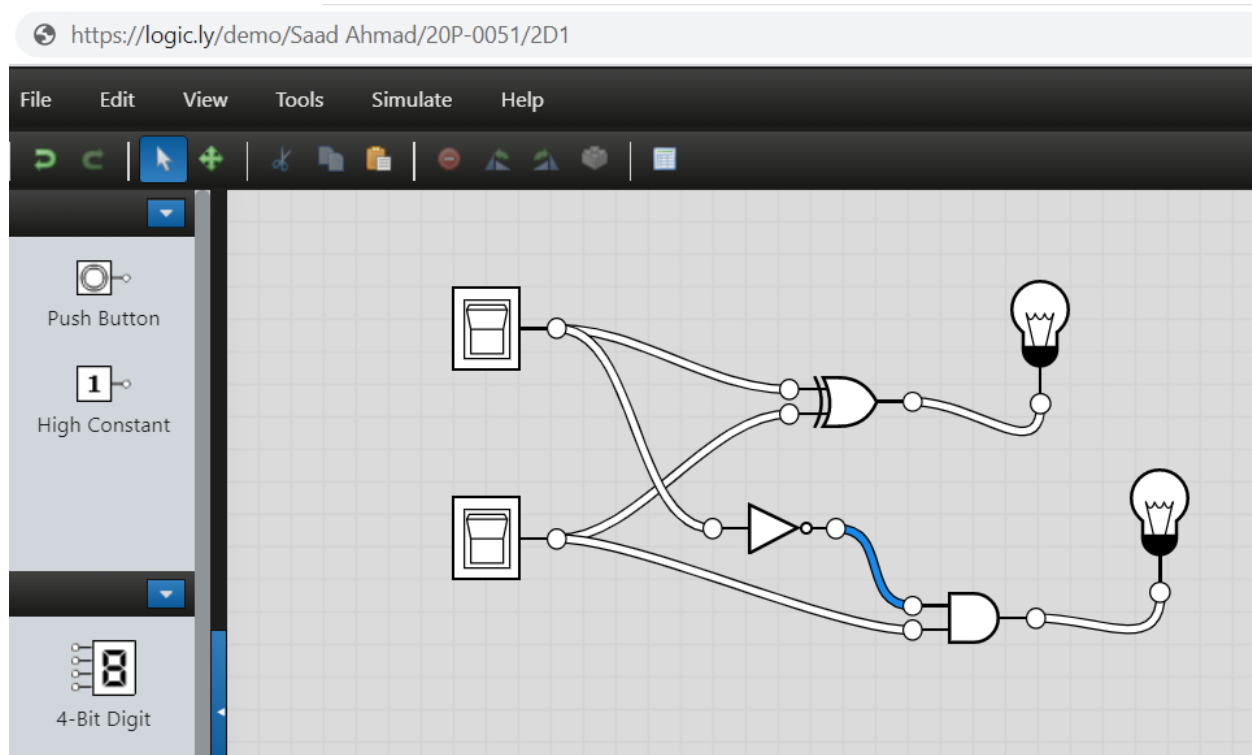

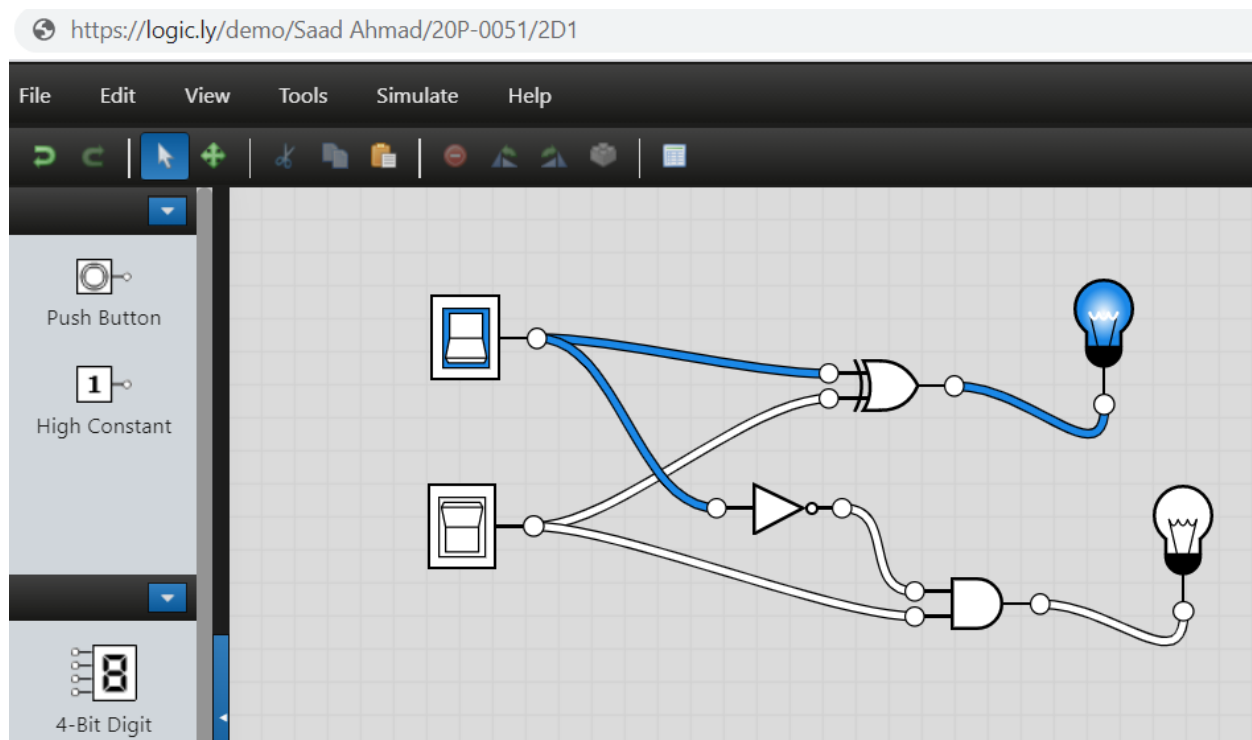d) Software Simulation (Show here your results for each combination that gives a high output)



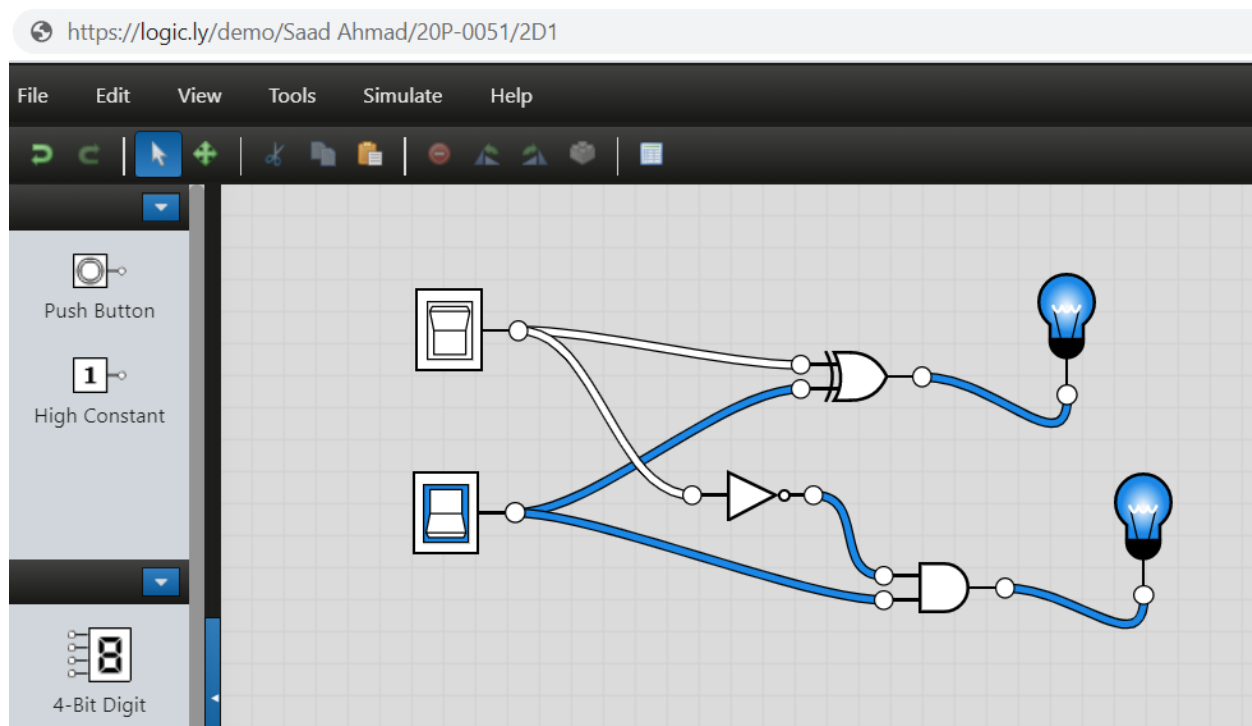

Full Subtractor

a) Truth Table

A	B	Borrow in	Difference	Borrow out
0	0	0	0	0
1	0	0	1	0
0	1	0	1	1
1	1	0	0	0
0	0	1	1	1
1	0	1	0	0
0	1	1	0	1
1	1	1	1	1

b) Boolean Expression (Simplified)


Difference:

$$D = (A \text{ X-OR } B) \text{ XOR } B_{IN} = (A \oplus B) \oplus B_{IN}$$



Borrow:



$$B_{OUT} = (\text{NOT } A \text{ AND } B) \text{ OR } \{\text{NOT } (A \text{ X-OR } B)\} B_{IN} = A'.B + \{(A \oplus B)\}'B_{IN}$$

c) Logic Diagram

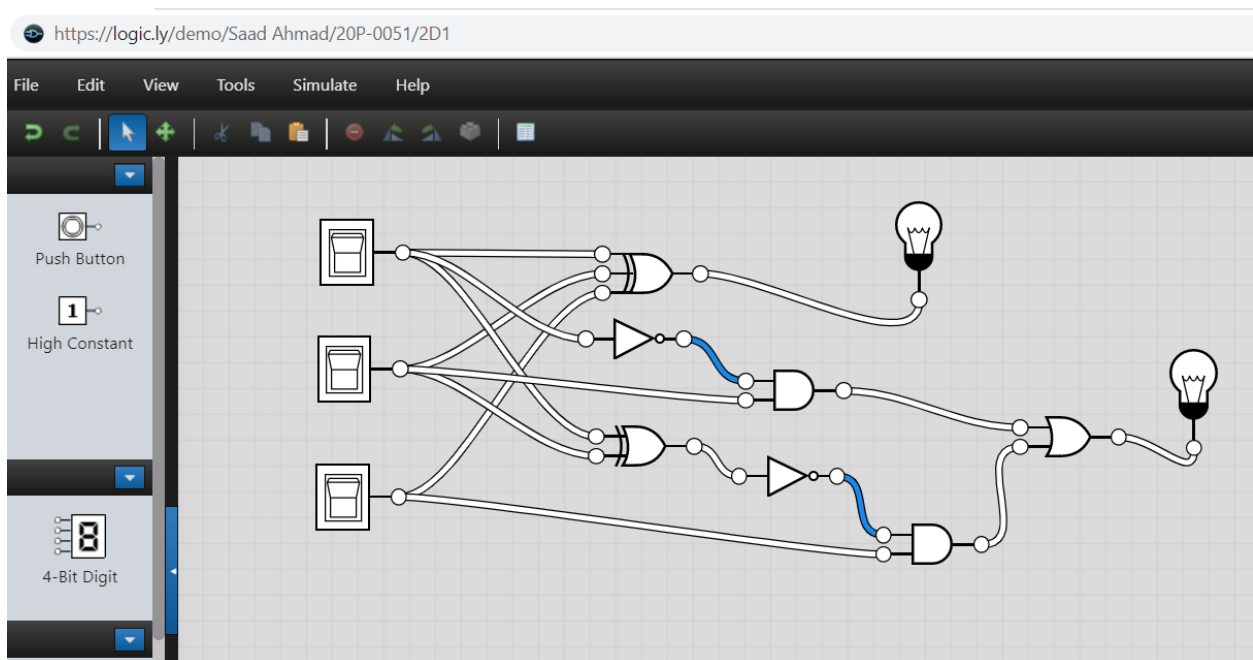

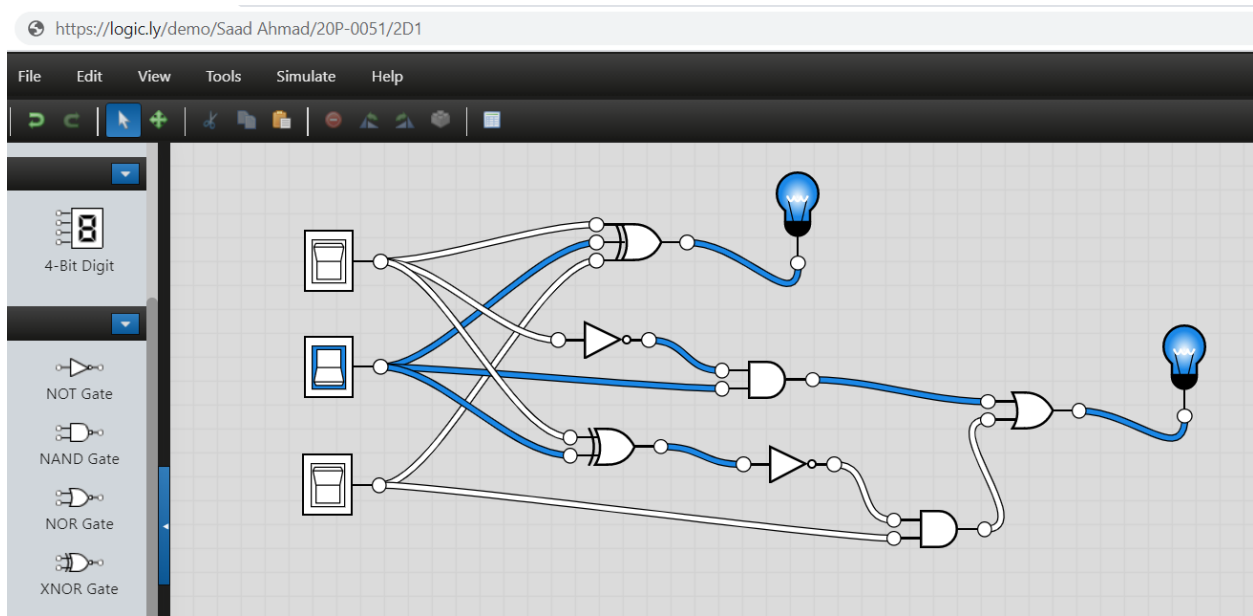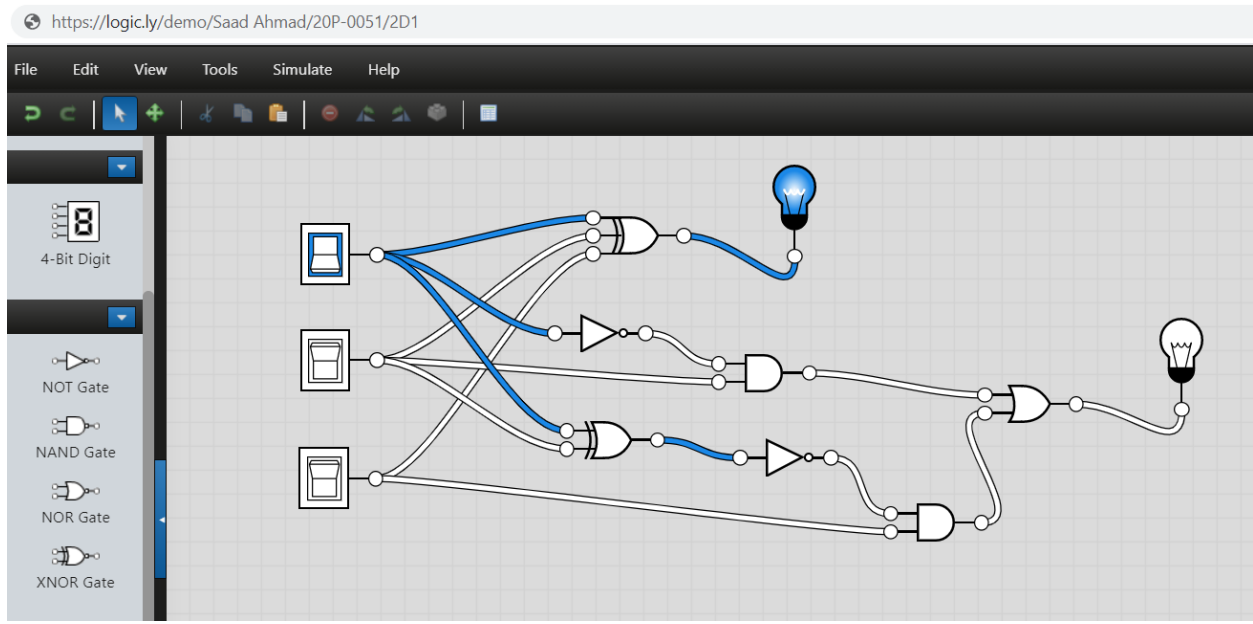- d) Software Simulation (Show here your results for each combination that gives a high output)




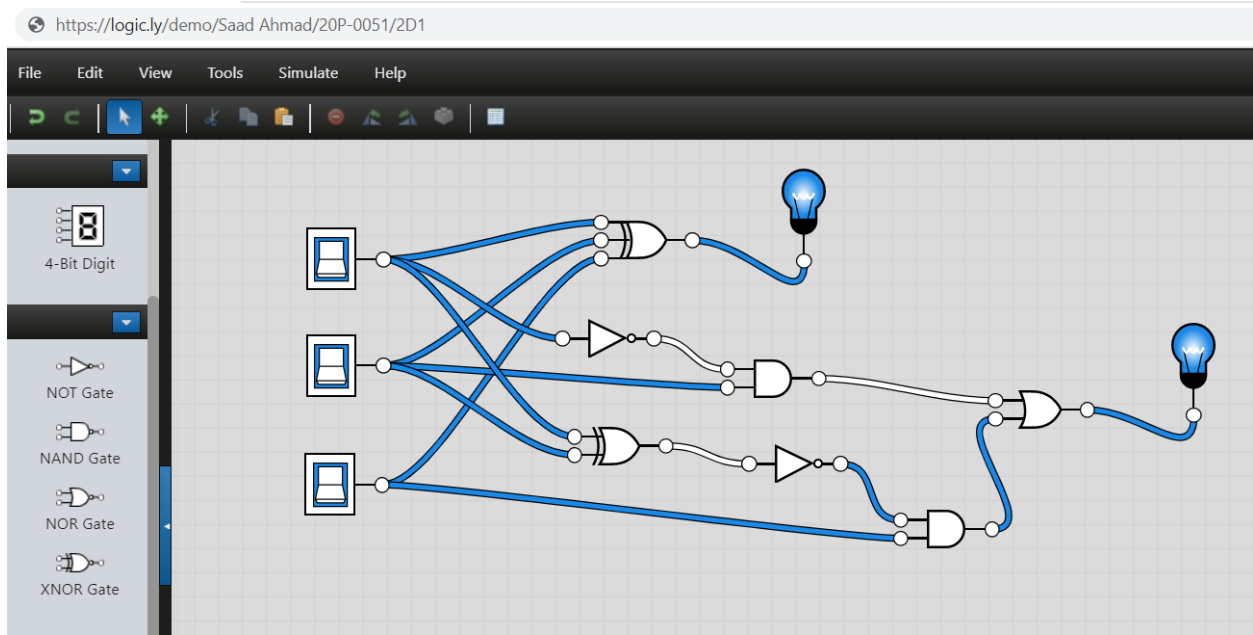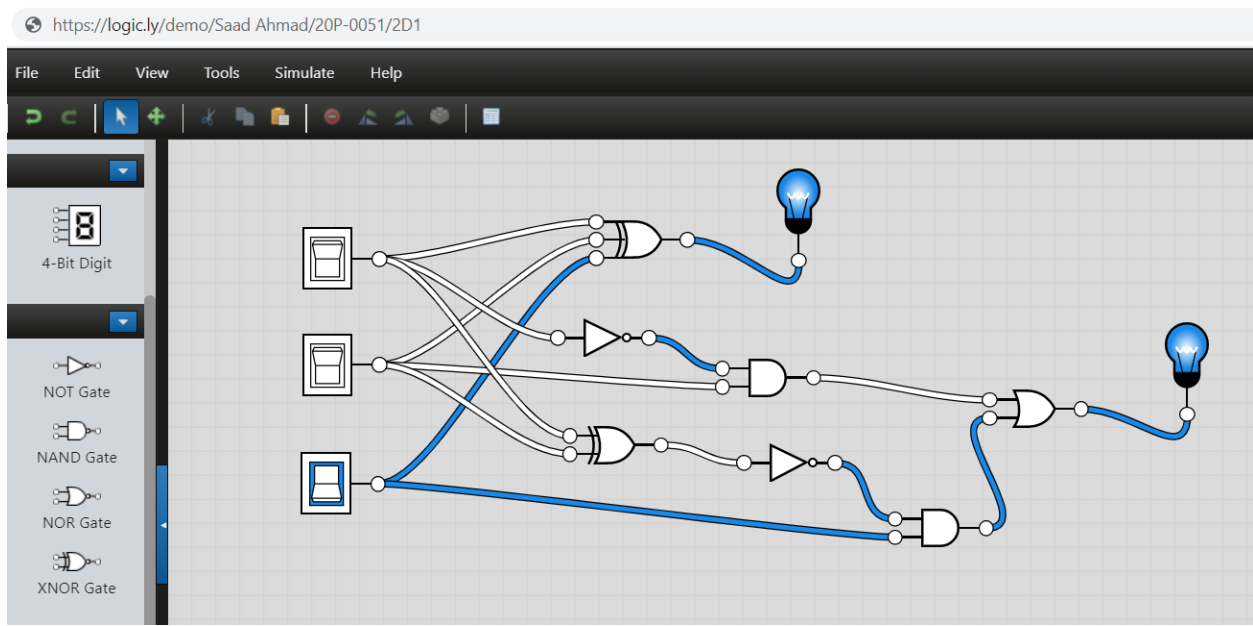

2. A full subtractor can be implemented using 2-half subtractors.

Demonstrate the logic diagram for the said circuit. Simulate your circuit for the verification of results.

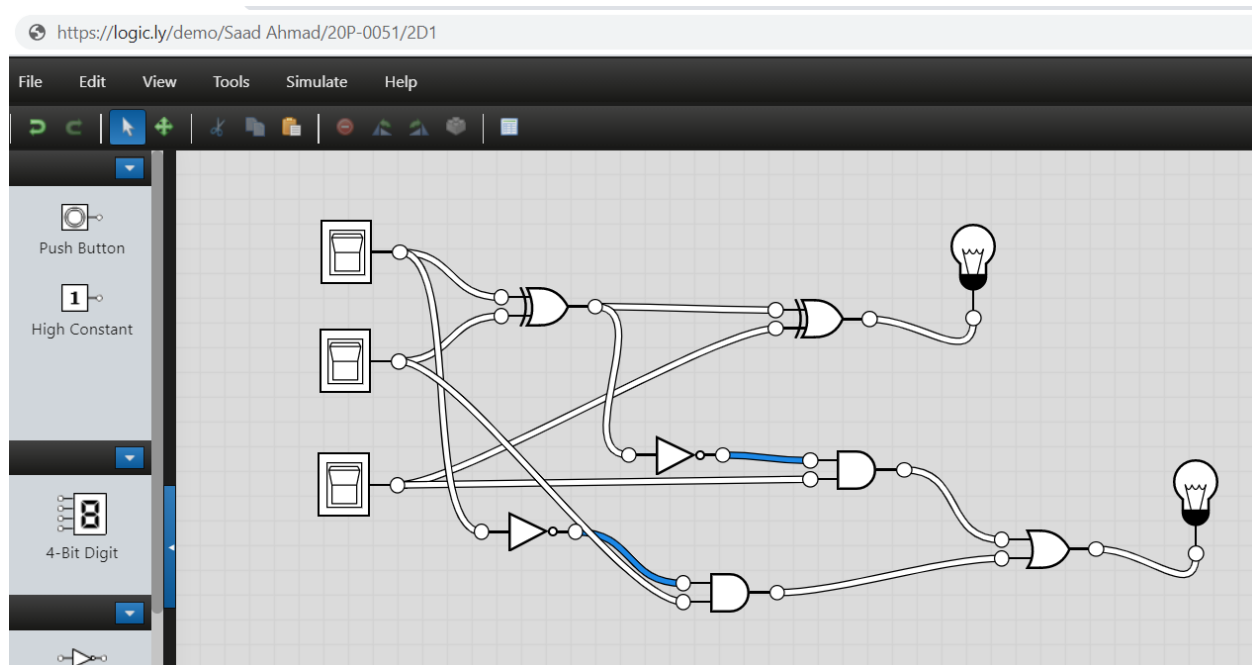a) Logic Diagram of Full Subtractor using 2-Half Subtractor



b) **Software Simulation** (Show here your results for each combination that gives a high output)

