

LAB 2

UNIVERSAL LOGIC GATES

Note: Make sure to give proper headings (as the one mentioned below) for each gate while making this lab report

Task 1

Simulate the logic gates (NOT, AND, OR, NOR, Ex-OR, Ex-NOR) using only NAND gates in Logically software.

Make a truth table and verify all the combinations for each of these gates. Paste the screenshots of your circuit (logic diagram) for each of above-mentioned gates having all the combinations. For example, if you make a NOT gate using NAND gate, simulate it for both of its possible combinations i.e. 0 and 1 and paste its screenshot (for both combinations).

NOT using NAND Gate

Task 2

Simulate the logic gates (NOT, AND, NAND, OR, Ex-OR, Ex-NOR) using only NOR gates in Logically software.

Make a truth table and verify all the combinations for each of these gates. Paste the screenshots of your circuit (logic diagram) for each of above-mentioned gates having all the combinations. For example, if you make a NOT gate using NOR gate, simulate it for both of its possible combinations i.e. 0 and 1 and paste its screenshot (for both combinations).